COMP278 MIDTERM REVIEW 2

| | NAME | |
|--------|--------------------------------------|---|
| Comp | olete this exam within 50 minutes. | Write legibly and check your work. Good luck! |
| | 1. Binary a | RITHMETIC (20%) |
| Perfor | rm the following basic arithmetic of | operations on binary numbers. |
| (1) | 10011111 +00011011 | |

$$\begin{array}{c} (2) & 10100 \\ -1011110 \end{array}$$

2. Number representation (20%)

Convert the following numbers to the specified bases:

(1) $(37673375316)_8$ in binary.

(2) The number above, $(37673375316)_8$, in hexadecimal.

(3) $(2471)_8$ in binary.

(4) The number above, $(2471)_8$, in decimal.

3. Combinational circuit design (60%)

Given a 4-bit binary number, produce the even parity code for that number. The output should just be the even parity bit (the number of true bits should be even).

- (1) To the left, draw the truth table for this *even parity* circuit. Label inputs as: A_3, A_2, A_1, A_0 . Label the output as: EvenParity.
- (2) To the right, write the Boolean expression for *EvenParity*, then simplify it.

(3) Draw the logic diagram for this circuit based on the simplified Boolean algebraic expression. Label inputs and outputs as in the truth table.

(4) Use DeMorgan's Law to derive $\overline{EvenParity} = OddParity.$